
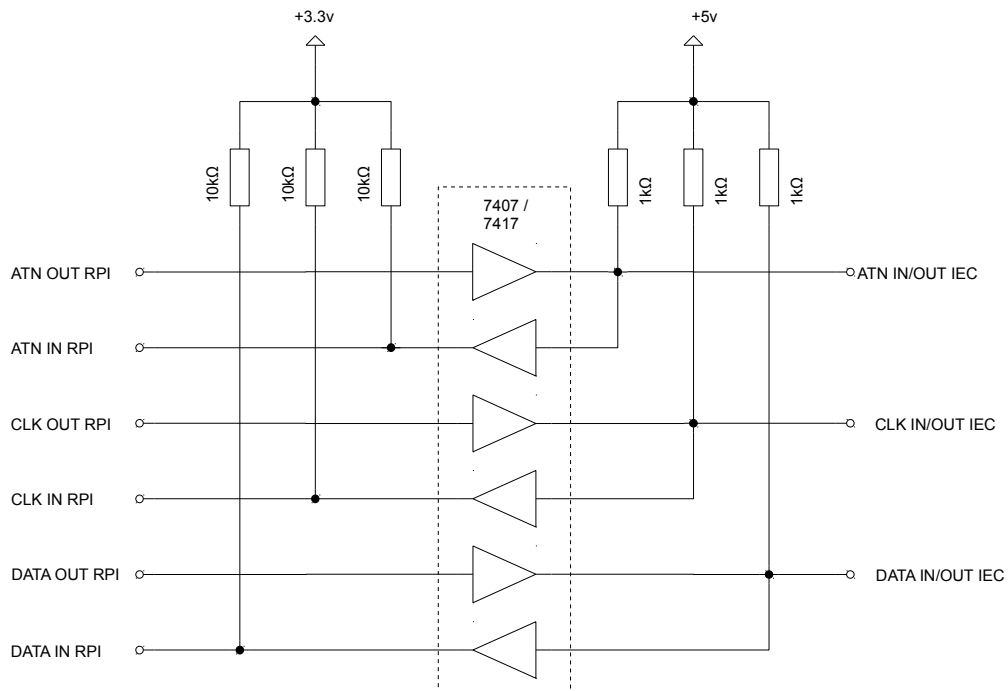


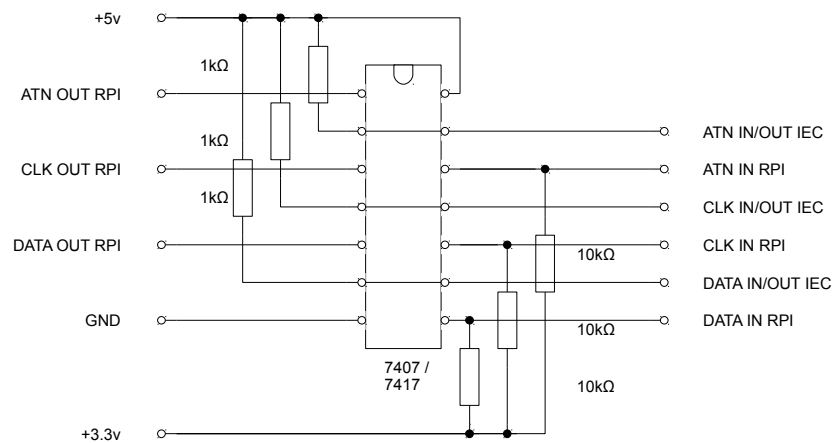
Circuit diagram of the Raspberry Pi GPIO <--> Commodore IEC adapter



Component layout of the adapter and connector pinouts




RASPBERRY PI P1 HEADER			
+3.3v	← 1	2	→ +5v
	3	4	
	5	6	
DEBUG1 (GPIO 4)	← 7	8	
GND	← 9	10	
ATN IN RPI (GPIO 17)	← 11	12	→ CLK IN RPI (GPIO 18)
DATA IN RPI (GPIO 27)	← 13	14	
ATN OUT RPI (GPIO 22)	← 15	16	→ CLK OUT RPI (GPIO 23)
	17	18	→ DATA OUT RPI (GPIO 24)
	19	20	
	21	22	→ DEBUG 2 (GPIO 25)
	23	24	
	25	26	

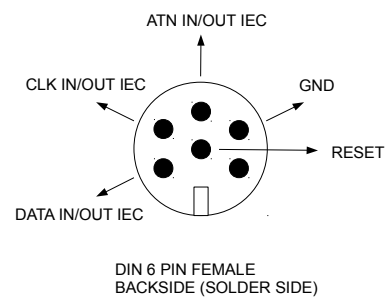


Assembling the adapter



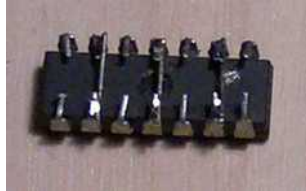
Start with the 7407 or 7417 open collector buffer.



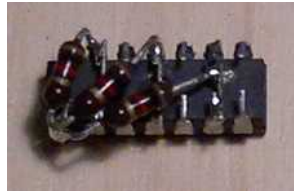
Connect pins 2-13, 4-11 and 6-9 with short jumper wires.




Then add the 1k resistors...

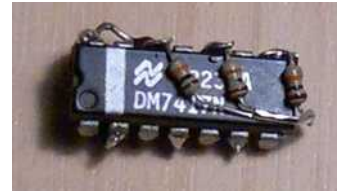

...and the 10k resistors...

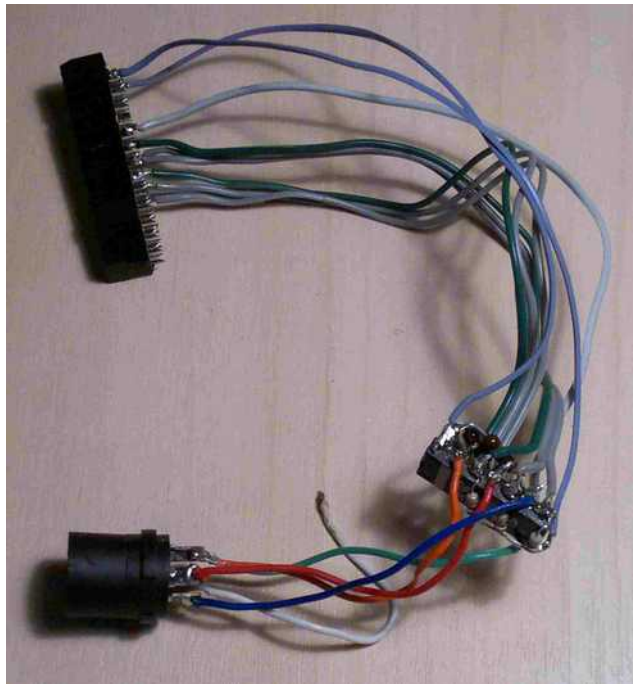

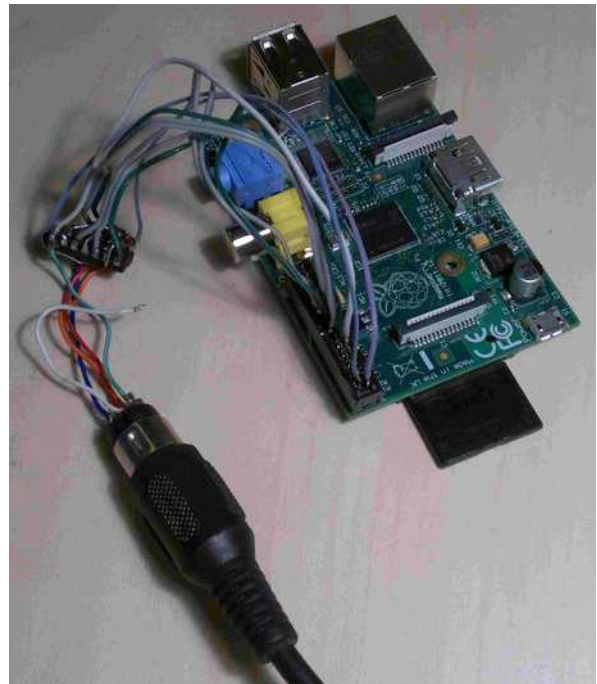...and finally all the wires to the connectors.



Perhaps not pretty but it works.